

OBJECTIVE:

Use 180 nm CMOS process with 1.8V power supply



- ① 40 dB DC Gain
- ② 100 MHz UGB
- ③ phase Margin should be better than 60° .


④ Output load = 1pF


⑤ Slew Rate : 10^6 V/s

⑥ Total current : 20 mA

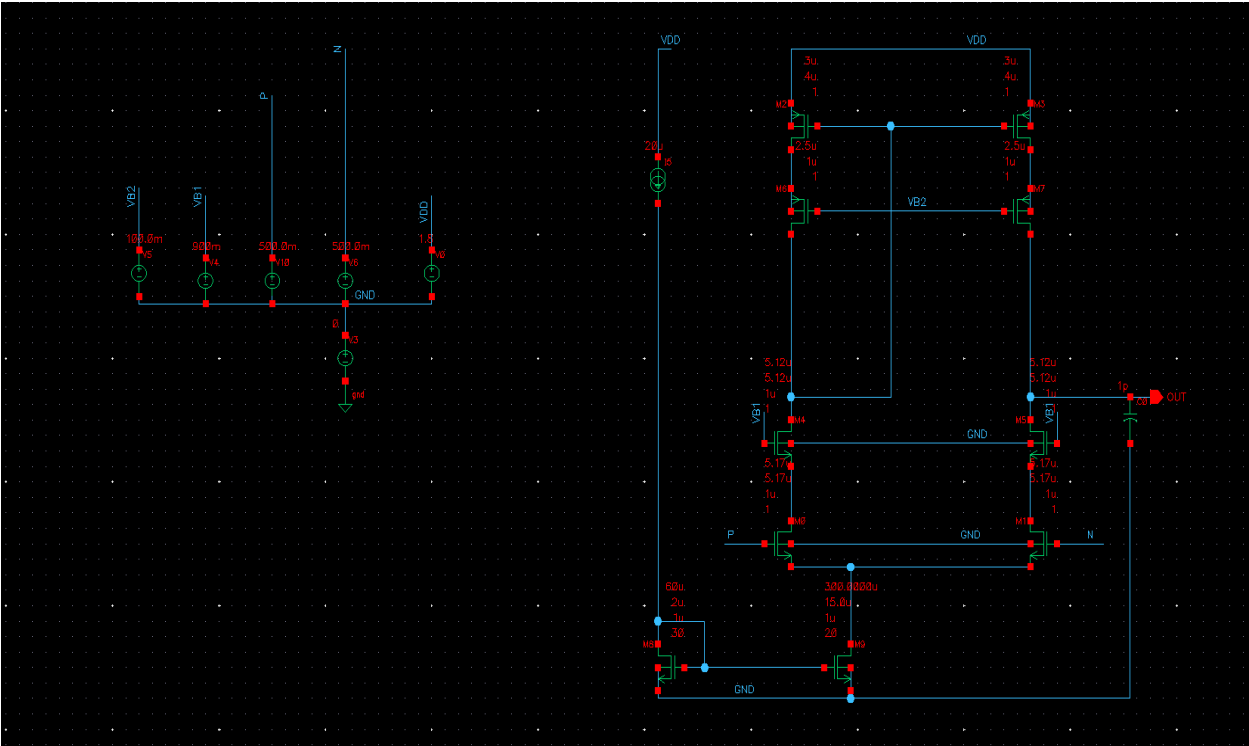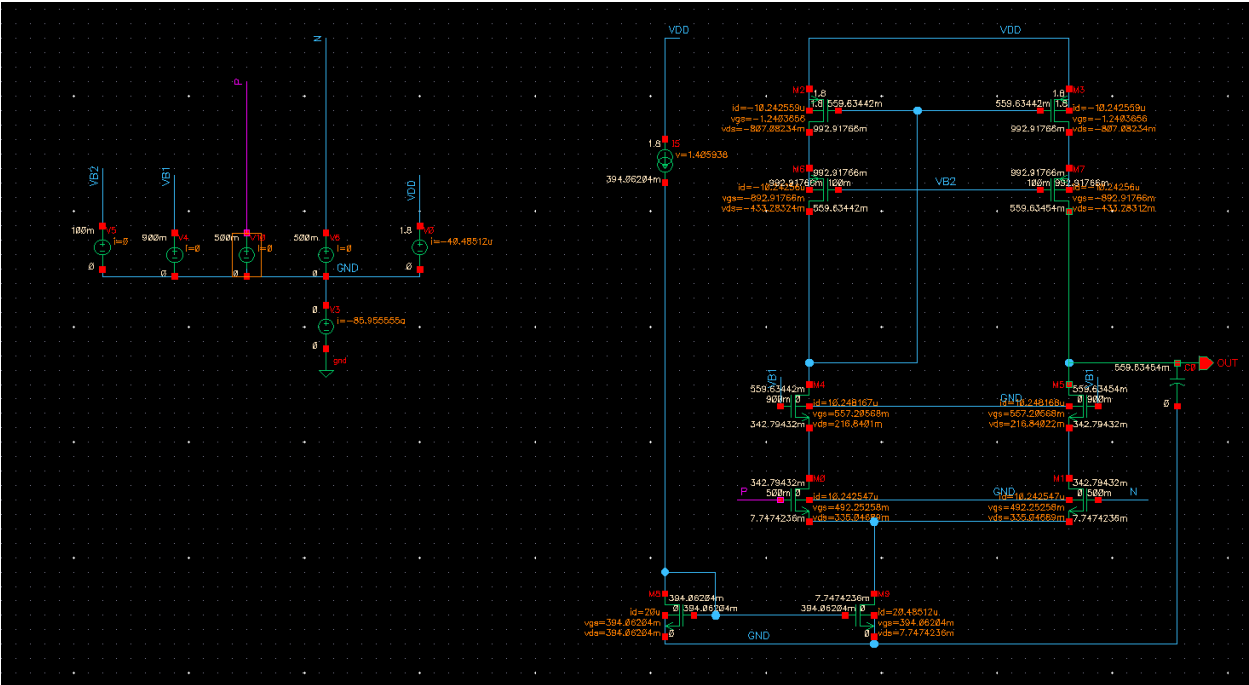You should also be able to achieve 84 dB SNR in 24 kHz BW.



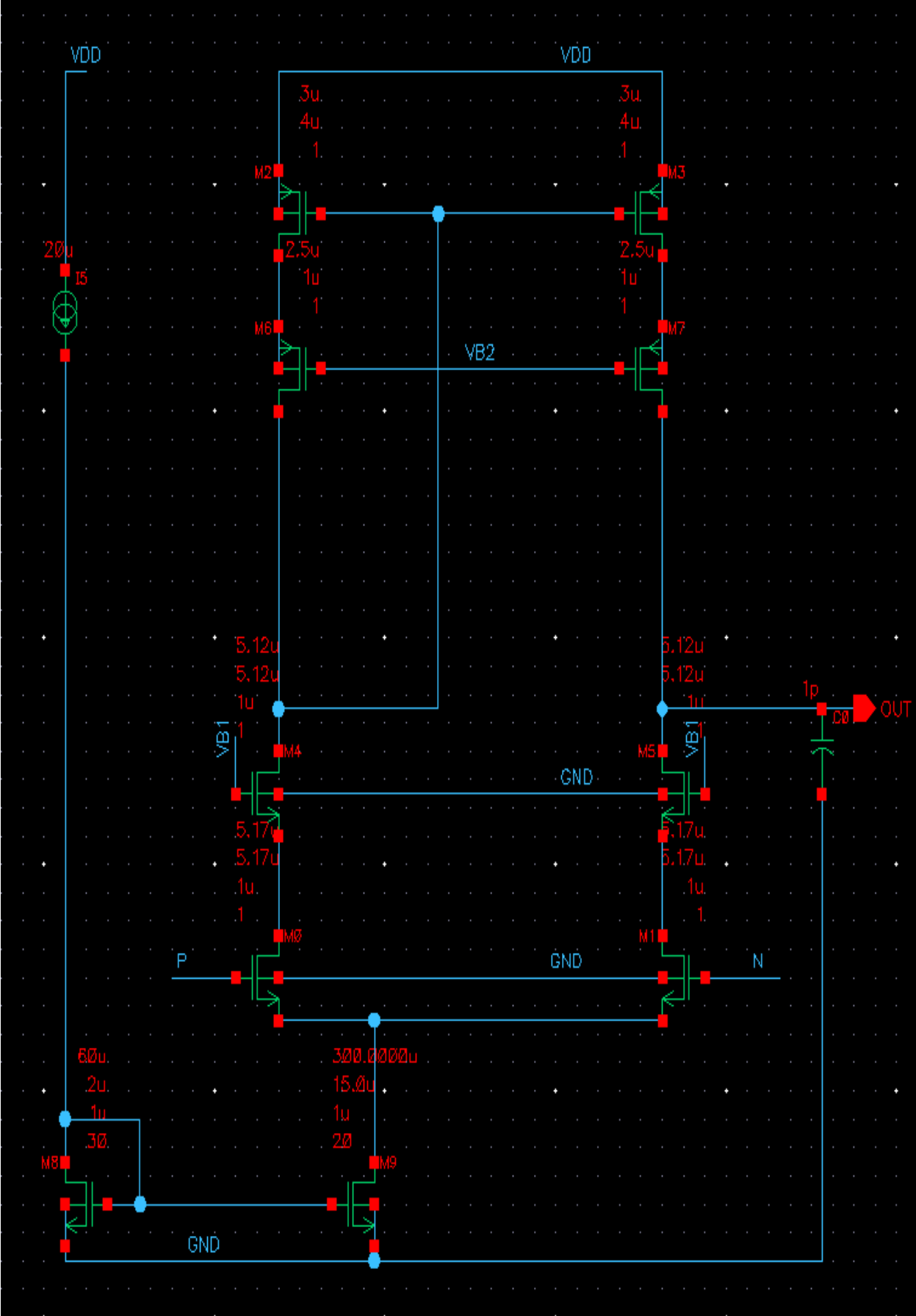

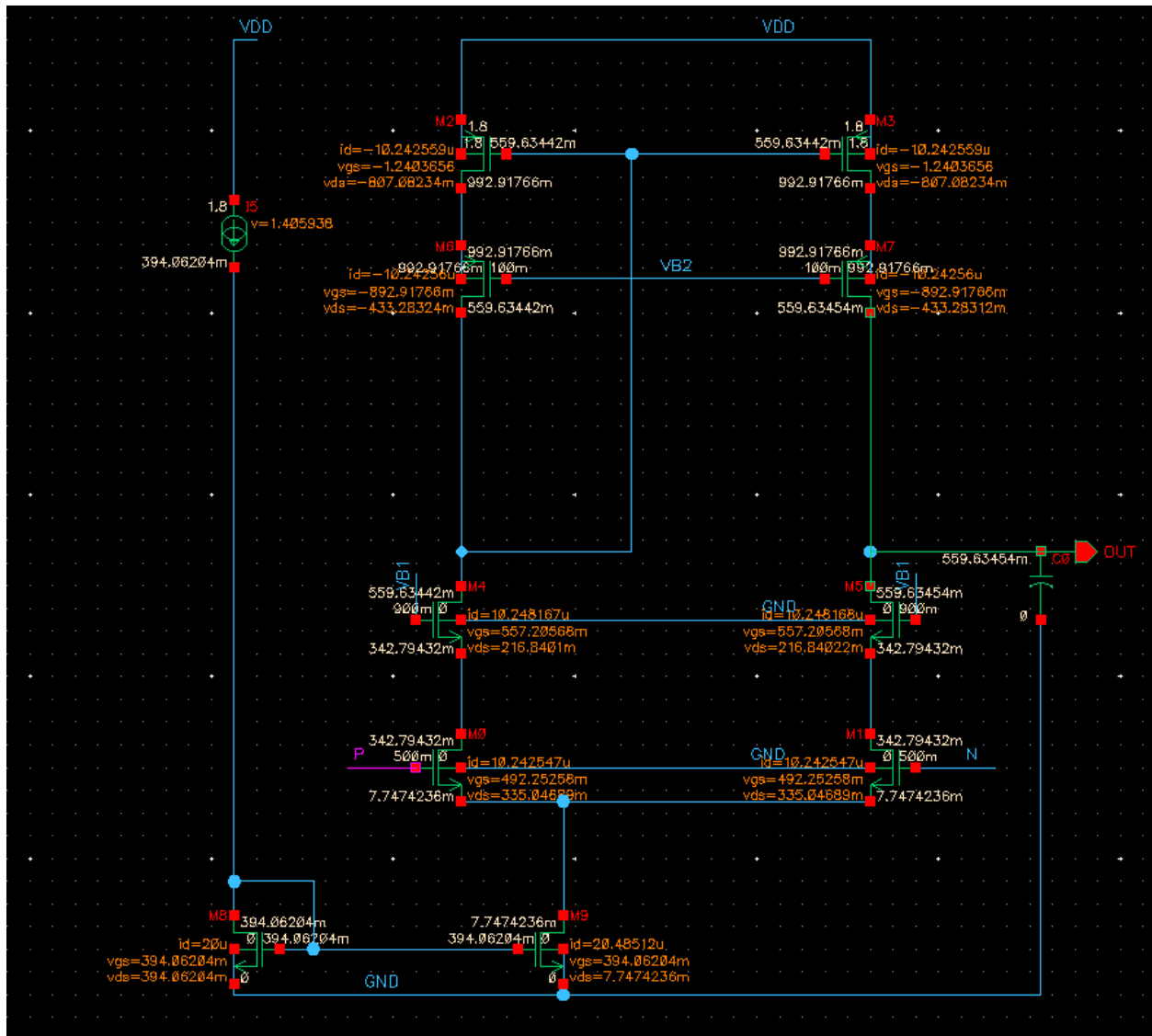

DC operation points in table for source

signal OP("/V5" "??")	signal OP("/V4" "??")	signal OP("/V10 " "??")	signal OP("/V1" "??")	signal OP("/V6 " "??")	signal OP("/V3 " "??")	signal OP("/V0 " "??")	signal OP("/I5" "??")
i 0	i 0	i 0	i 0	i 0	i - 86.69760 8a	i - 40.48512 u	i 20u
pwr 0	pwr 0	pwr 0	pwr 0	pwr 0	pwr -0	pwr - 72.87321 5u	pwr 28.11875 9u
v 100m	v 900m	v 500m	v 0	v 500m	v 0	v 1.8	v 1.405938

DC operation points in table for mosfet

signal OP("/ M8" "??")	signal OP("/ M0" "??")	signal OP("/ M4" "??")	signal OP("/ M2" "??")	signal OP("/ M6" "??")	signal OP("/ M9" "??")	signal OP("/ M7" "??")	signal OP("/ M3" "??")	signal OP("/ M1" "??")	signal OP("/ M5" "??")	signa l OP("/ C0" "??")
beff 20.30 2713	beff 1.932 0107 m	beff 1.963 2637 m	beff 34.53 7545u	beff 131.4 9723u	beff 994.2 1028 m	beff 131.4 9724u	beff 34.53 7545u	beff 1.932 0107 m	beff 1.963 2637 m	cap 1p
betaef f 17.78 38m	betaef f 1.541 4003 m	betaef f 1.535 164m	betaef f 38.59 6582u	betaef f 141.9 5031u	betaef f 89.29 5248 m	betaef f 141.9 5031u	betaef f 38.59 6582u	betaef f 1.541 4003 m	betaef f 1.535 164m	
fug 239.9 3393 M	fug 627.3 1035 M	fug 636.4 2508 M	fug 49.22 4494 M	fug 431.0 5342 M	fug 31.39 254M	fug 431.0 5348 M	fug 49.22 4494 M	fug 627.3 1035 M	fug 636.4 2494 M	
gbd 0	gbd 0	gbd 0	gbd 0	gbd 0	gbd 0	gbd 0	gbd 0	gbd 0	gbd 0	
gbs 3.291 6086n	gbs 0	gbs 0	gbs 26.39 7284p	gbs 26.62 6759p	gbs 2.183 5416n	gbs 26.62 6759p	gbs 26.39 7284p	gbs 0	gbs 0	
gds 4.929 9058u	gds 2.043 1925u	gds 3.779 4728u	gds 396.2 3793n	gds 1.755 531u	gds 2.467 7082 m	gds 1.755 525u	gds 396.2 3789n	gds 2.043 1924 u	gds 3.779 4831u	
gm 428.0 8276u	gm 140.4 2947u	gm 140.3 2877u	gm 23.93 7259u	gm 45.10 6832u	gm 332.6 6005u	gm 45.10 6837u	gm 23.93 7259u	gm 140.4 2947 u	gm 140.3 2874u	
gmb 89.27 7278u	gmb 28.44 6505u	gmb 23.75 6101u	gmb 8.330 0695u	gmb 14.29 5062u	gmb 71.48 4779u	gmb 14.29 5064u	gmb 8.330 0695u	gmb 28.44 6505 u	gmb 23.75 6096u	
gmbs 89.27 7278u	gmbs 28.44 6505u	gmbs 23.75 6101u	gmbs 8.330 0695u	gmbs 14.29 5062u	gmbs 71.48 4779u	gmbs 14.29 5064u	gmbs 8.330 0695u	gmbs 28.44 6505 u	gmbs 23.75 6096u	


gmove rid 21.40 4138	gmov erid 13.71 0406	gmov erid 13.69 306	gmov erid 2.337 039	gmove rid 4.403 863	gmov erid 16.23 9107	gmov erid 4.403 8635	gmov erid 2.337 039	gmov erid 13.71 0406	gmove rid 13.69 306
i1 20u	i1 10.24 2547u	i1 10.24 8167u	i1 - 10.24 2559u	i1 - 10.24 256u	i1 20.48 512u	i1 - 10.24 256u	i1 - 10.24 2559u	i1 10.24 2547 u	i1 10.24 8166u
i3 -20u	i3 - 10.24 2547u	i3 - 10.24 8167u	i3 10.24 2559u	i3 10.24 256u	i3 - 20.48 5119u	i3 10.24 256u	i3 10.24 2559u	i3 - 10.24 2547 u	i3 - 10.24 8166u
i4 - 9.735 2183f	i4 - 2.214 7459f	i4 - 2.195 1751f	i4 594.2 0836a	i4 575.2 3892a	i4 - 30.72 9917f	i4 575.2 3892a	i4 594.2 0836a	i4 - 2.214 7459f	i4 - 2.195 1751f
ib NaN	ib NaN	ib NaN	ib NaN	ib NaN	ib NaN	ib NaN	ib NaN	ib NaN	ib NaN
id 20u	id 10.24 2547u	id 10.24 8167u	id - 10.24 2559u	id - 10.24 256u	id 20.48 512u	id - 10.24 256u	id - 10.24 2559u	id 10.24 2547 u	id 10.24 8166u
idb 7.453 0363f	idb 1.107 3729f	idb 1.097 5875f	idb 406.7 4783a	idb 348.3 3075a	idb 30.41 9789f	idb 348.3 3075a	idb 406.7 4783a	idb 1.107 3729f	idb 1.097 5875f
ide 20u	ueff 34.90 6736 m	ide 10.24 8168u	ide - 10.24 2561u	ide - 10.24 2561u	ide 20.48 512u	ide - 10.24 2561u	ide - 10.24 2561u	ide 10.24 2547 u	ide 10.24 8166u
ids 20u	ids 10.24 2547u	ids 10.24 8167u	ids - 10.24 2559u	ids - 10.24 256u	ids 20.48 5119u	ids - 10.24 256u	ids - 10.24 2559u	ids 10.24 2547 u	ids 10.24 8166u
is -20u	is - 10.24 2547u	is - 10.24 8167u	is 10.24 2559u	is 10.24 256u	is - 20.48 5119u	is 10.24 256u	is 10.24 2559u	is - 10.24 2547 u	is - 10.24 8166u
isb 2.282 182f	isb 1.107 3729f	isb 1.097 5875f	isb 187.4 6053a	isb 226.9 0817a	isb 310.1 2876a	isb 226.9 0817a	isb 187.4 6053a	isb 1.107 3729f	isb 1.097 5875f
ise 20u	ise 10.24 2547u	ise 10.24 8168u	ise - 10.24 2559u	ise - 10.24 256u	ise 20.48 512u	ise - 10.24 256u	ise - 10.24 2559u	ise 10.24 2547 u	ise 10.24 8166u

isub 0	isub 0	isub 0	isub -0	isub -0	isub 0	isub -0	isub -0	isub 0	isub 0
pwr 7.881 2407u	pwr 3.431 7335u	pwr 2.222 2136u	pwr 8.266 5886u	pwr 4.437 9297u	pwr 158.7 069n	pwr 4.437 9329u	pwr 8.266 5887u	pwr 3.431 7335 u	pwr 2.222 2099u
region 2	region 2	region 2	region 2	region 2	region 2	region 2	region 2	regio n 2	region 2
ron 19.70 3103K	ron 32.71 1288 K	ron 21.15 8915 K	ron 78.79 6943 K	ron 42.30 224K	ron 378.1 9763	ron 42.30 227K	ron 78.79 6944 K	ron 32.71 1288 K	ron 21.15 8886K
rout 202.8 4363K	rout 489.4 3015 K	rout 264.5 8717 K	rout 2.523 7362 M	rout 569.6 2822K	rout 405.2 343	rout 569.6 3017 K	rout 2.523 7364 M	rout 489.4 3016 K	rout 264.5 8645K
self_g ain 86.83 3862	self_g ain 68.73 0419	self_g ain 37.12 9192	self_g ain 60.41 1328	self_g ain 25.69 4124	self_g ain 134.8 0527 m	self_g ain 25.69 4215	self_g ain 60.41 1333	self_g ain 68.73 042	self_g ain 37.12 9084
type 0	type 0	type 0	type 1	type 1	type 0	type 1	type 1	type 0	type 0
ueff 34.86 5931 m	ueff 34.90 6736 m	ueff 35.10 5997 m	ueff 5.718 1809 m	ueff 6.212 4729 m	ueff 34.78 4537 m	ueff 6.212 4729 m	ueff 5.718 1809 m	ueff 34.90 6736 m	ueff 35.10 5997 m
vbs 0	vbs - 7.747 4236 m	vbs - 342.7 9432 m	vbs 0	vbs 0	vbs 0	vbs 0	vbs 0	vbs - 7.747 4236 m	vbs - 342.7 9432 m
vdb 394.0 6204 m	vdb 342.7 9432 m	vdb 559.6 3442 m	vdb - 807.0 8234 m	vdb - 433.2 8324 m	vdb 7.747 4236 m	vdb - 433.2 8355 m	vdb - 807.0 8236 m	vdb 342.7 9432 m	vdb 559.6 3409 m
vds 394.0 6204 m	vds 335.0 4689 m	vds 216.8 401m	vds - 807.0 8234 m	vds - 433.2 8324 m	vds 7.747 4236 m	vds - 433.2 8355 m	vds - 807.0 8236 m	vds 335.0 469m	vds 216.8 3977 m


vdsat 64.10 5226 m	vdsat 119.6 9808 m	vdsat 123.4 1071 m	vdsat - 656.5 5699 m	vdsat - 357.8 6091 m	vdsat 66.56 5876 m	vdsat - 357.8 609m	vdsat - 656.5 5699 m	vdsat 119.6 9808 m	vdsat 123.4 1071 m
vdss 64.10 5226 m	vdss 119.6 9808 m	vdss 123.4 1071 m	vdss - 656.5 5699 m	vdss - 357.8 6091 m	vdss 66.56 5876 m	vdss - 357.8 609m	vdss - 656.5 5699 m	vdss 119.6 9808 m	vdss 123.4 1071 m
vearly 4.056 8727	vearly 5.013 0115	vearly 2.711 5338	vearly 25.84 9521	vearly 5.834 4519	vearly 8.301 2731 m	vearly 5.834 4718	vearly 25.84 9523	vearly y 5.013 0116	vearly 2.711 5259
vfbeff - 934.2 2806 m	vfbeff - 938.7 5343 m	vfbeff - 935.9 9979 m	vfbeff - 993.6 5101 m	vfbeff - 967.0 875m	vfbeff - 942.2 0662 m	vfbeff - 967.0 875m	vfbeff - 993.6 5101 m	vfbeff - 938.7 5343 m	vfbeff - 935.9 9979 m
vgb 394.0 6204 m	vgb 500m	vgb 900m	vgb - 1.240 3656	vgb - 892.9 1766 m	vgb 394.0 6204 m	vgb - 892.9 1764 m	vgb - 1.240 3656	vgb 500m	vgb 900m
vgd 0	vgd 157.2 0568 m	vgd 340.3 6558 m	vgd - 433.2 8324 m	vgd - 459.6 3442 m	vgd 386.3 1462 m	vgd - 459.6 3409 m	vgd - 433.2 8323 m	vgd 157.2 0568 m	vgd 340.3 6591 m
vgs 394.0 6204 m	vgs 492.2 5258 m	vgs 557.2 0568 m	vgs - 1.240 3656	vgs - 892.9 1766 m	vgs 394.0 6204 m	vgs - 892.9 1764 m	vgs - 1.240 3656	vgs 492.2 5258 m	vgs 557.2 0568 m
vgstef f 33.76 9836 m	vgstef f 108.2 6443 m	vgstef f 107.3 869m	vgstef f 770.1 0308 m	vgstef f 394.4 1728 m	vgstef f 36.38 7144 m	vgstef f 394.4 1727 m	vgstef f 770.1 0308 m	vgstef f 108.2 6443 m	vgstef f 107.3 869m
vgt 1.403 631m	vgt 102.9 7083 m	vgt 102.1 7598 m	vgt - 770.1 4684 m	vgt - 394.6 9441 m	vgt 6.419 4102 m	vgt - 394.6 944m	vgt - 770.1 4684 m	vgt 102.9 7083 m	vgt 102.1 7597 m

vsat_ marg 329.9 5682 m	vsat_ marg 215.3 4882 m	vsat_ marg 93.42 9384 m	vsat_ marg - 150.5 2536 m	vsat_ marg - 75.42 2334 m	vsat_ marg - 58.81 8452 m	vsat_ marg - 75.42 2655 m	vsat_ marg - 150.5 2537 m	vsat_ marg 215.3 4882 m	vsat_marg 93.429063m
vth 392.6 5841 m	vth 389.2 8174 m	vth 455.0 2971 m	vth - 470.2 1875 m	vth - 498.2 2325 m	vth 387.6 4263 m	vth - 498.2 2325 m	vth - 470.2 1875 m	vth 389.2 8174 m	vth 455.0 2971 m

Q2

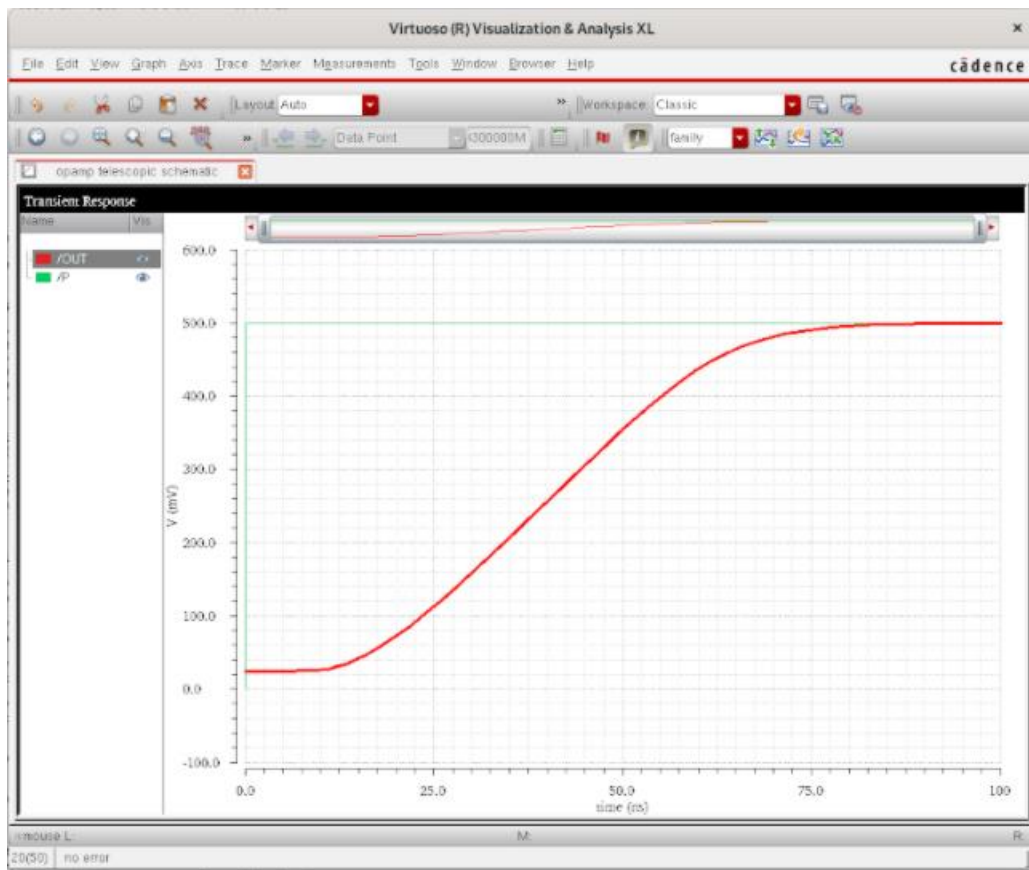

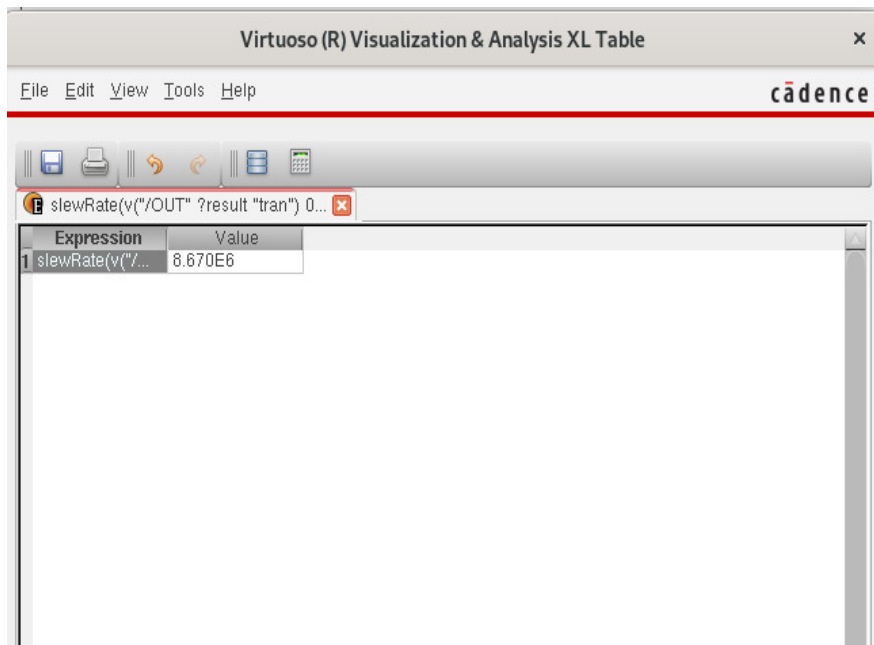Connect negative and output terminal and connect positive terminal to Vpsule




Slew rate is 8.67E6 (V/s)

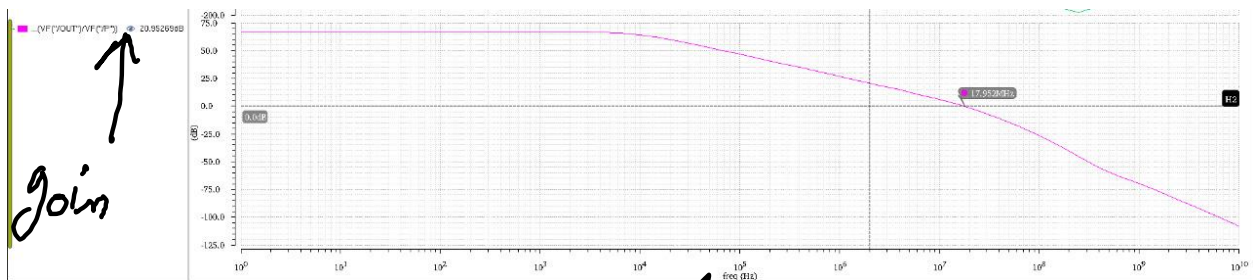
Q3

So gain is 67.23dB for this telescopic op-amp with phase margin of 53 degree and Unity gain

Bandwidth is 18Mhz. Results are displayed at bottom.




→ *freq*

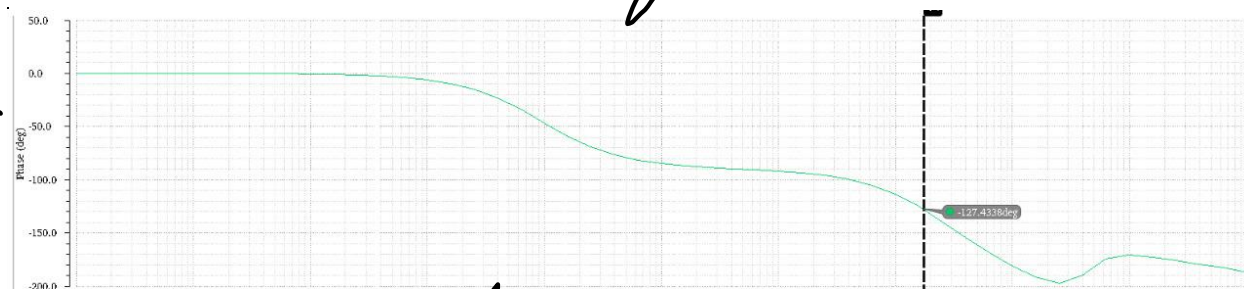

freq →

AC Response

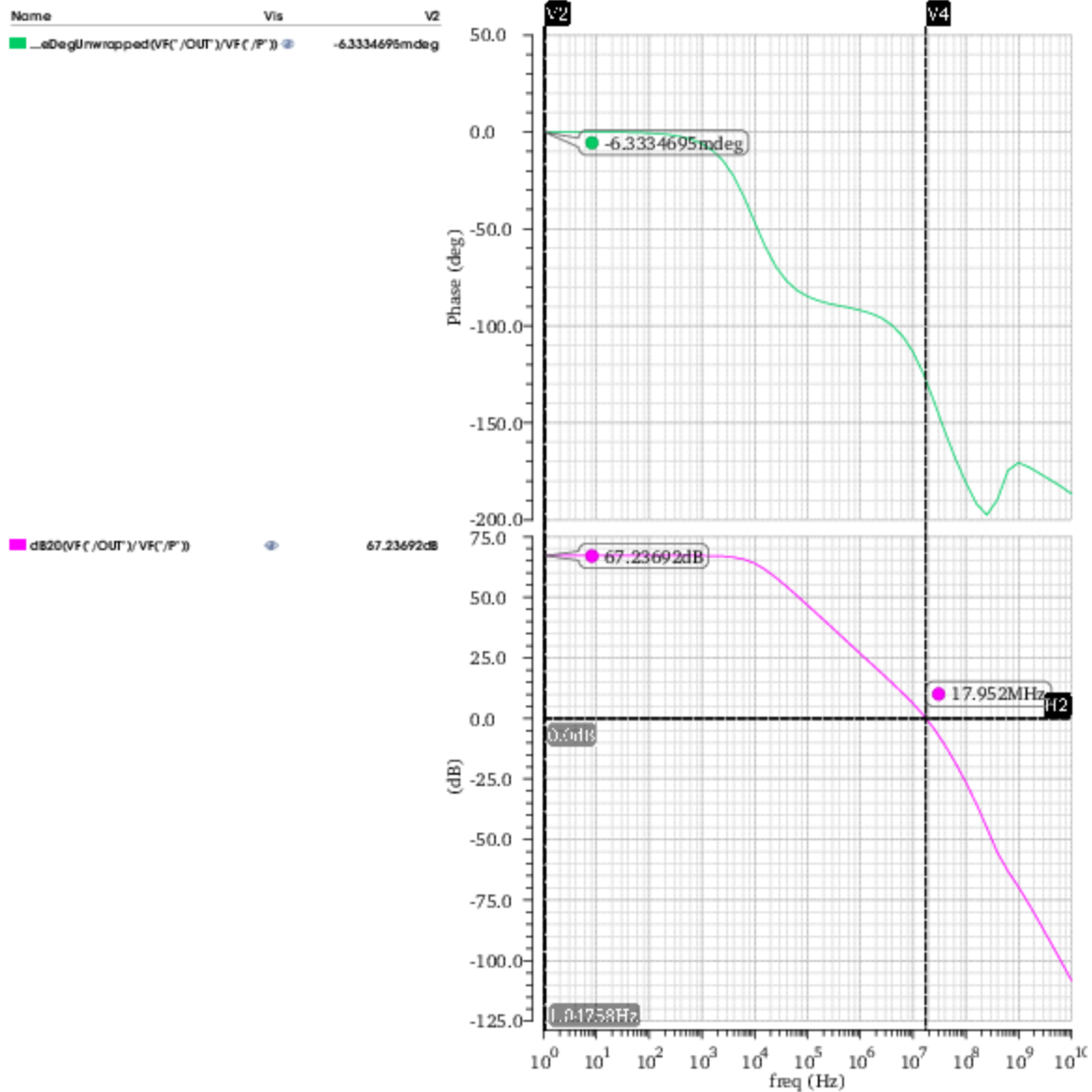

Markers

	V4	V1	V2
x	17.4147MHz	658.119mHz	1.04758Hz
phaseDegUnwrapped(VF('OUT')/VF('P'))	-127.4338deg	None	-6.333469mdeg
dB20(VF('OUT')/VF('P'))	324.9084m dB	None	67.23692dB

we have


$$PM = 180 - 127.43 \approx 52^\circ$$

Q5

Device	Param	Noise Contribution	% Of Total
/M1	fn	0.00164795	47.51
/M0	fn	0.00164062	47.30
/M3	fn	8.38505e-05	2.42
/M2	fn	8.3427e-05	2.41
/M1	id	5.32333e-06	0.15
/M0	id	5.29967e-06	0.15
/M3	id	8.97469e-07	0.03
/M2	id	8.92936e-07	0.03
/M5	fn	2.42637e-07	0.01
/M4	fn	2.41558e-07	0.01
/M7	fn	2.84038e-08	0.00
/M6	fn	2.82603e-08	0.00
/M5	id	7.84301e-10	0.00
/M4	id	7.80815e-10	0.00
/M1	rs	5.97298e-10	0.00
/M0	rs	5.94643e-10	0.00
/M7	id	1.10354e-10	0.00
/M6	id	1.09796e-10	0.00
/M3	rs	3.78855e-11	0.00
/M2	rs	3.76942e-11	0.00
/M8	fn	1.03822e-11	0.00
/M9	fn	2.3769e-12	0.00
/M9	id	2.18131e-12	0.00
/M8	id	1.68813e-13	0.00
/M5	rs	8.61884e-14	0.00
/M4	rs	8.58054e-14	0.00
/M1	rd	8.53549e-14	0.00
/M0	rd	8.49755e-14	0.00
/M7	rs	1.13944e-14	0.00
/M6	rs	1.13369e-14	0.00
/M3	rd	5.57521e-15	0.00
/M2	rd	5.54704e-15	0.00
/M9	rs	7.1066e-17	0.00
/M9	rd	5.24717e-17	0.00
/M5	rd	4.36968e-17	0.00
/M4	rd	4.35024e-17	0.00
/M7	rd	9.38938e-18	0.00
/M6	rd	9.34194e-18	0.00

/M8	rs	6.93635e-18	0.00
/M8	rd	6.17996e-22	0.00
Integrated Noise Summary (in V ²) Sorted By Noise Contributors			
Total Summarized Noise = 0.0034688			
Total Input Referred Noise = 7.56386e-10			
The above noise summary info is for noise data			

Q4

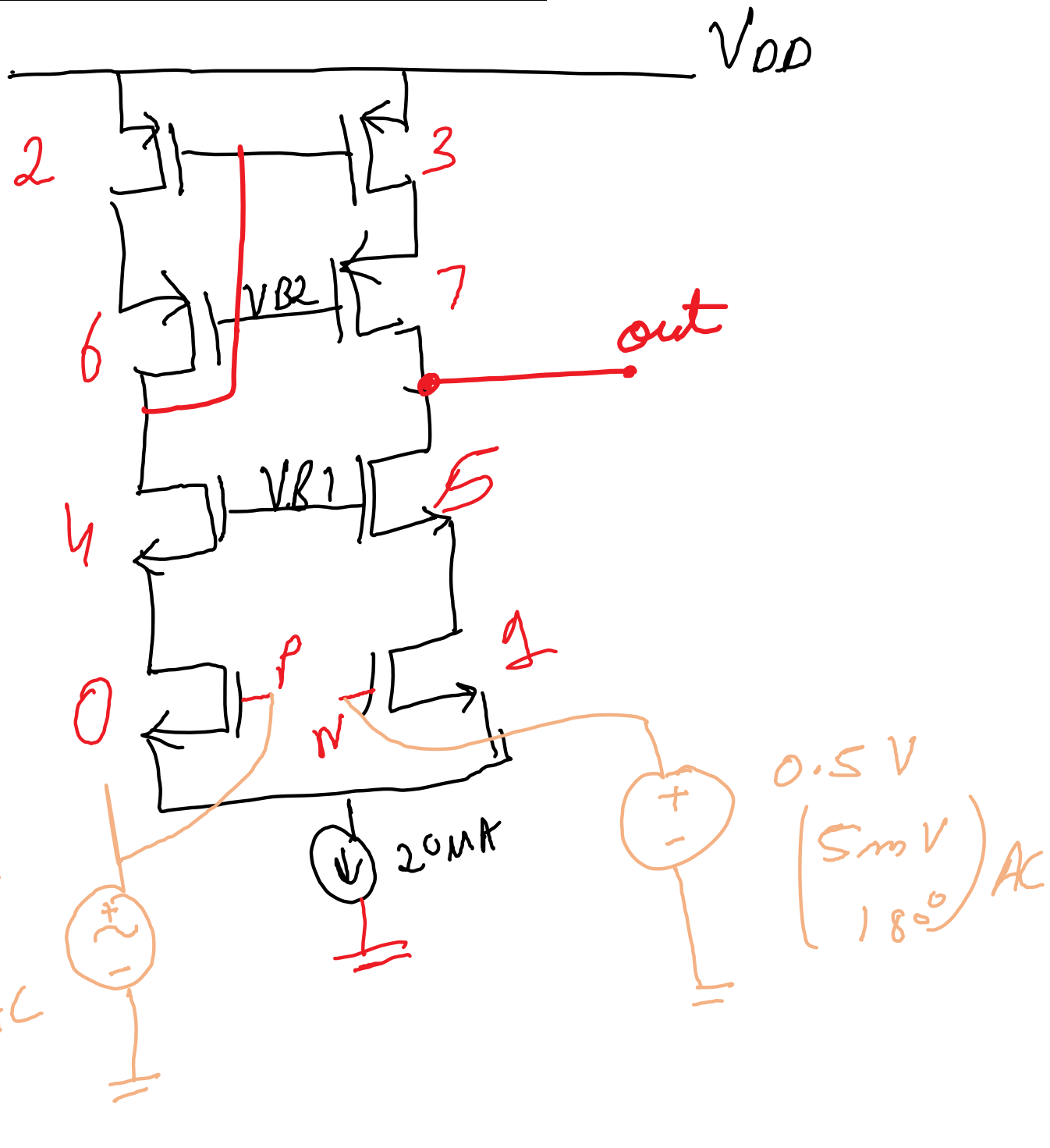

for (0 and 1)

$$V_{gs} = 0.5V, V_{th} = 0.392V$$


$$\beta_{eff} = \mu_m \frac{W}{L} = 17.78m$$

$$\text{So } I_D = \frac{1}{2} \times 17.78m \times (0.5 - 0.392)^2$$

$$= 10.38 \mu$$

$$\textcircled{1} g_{oh} = g_{m0} [g_{m5} r_{ds5} r_{ds1}] \times [g_{m7} r_{ds7} r_{ds}]$$
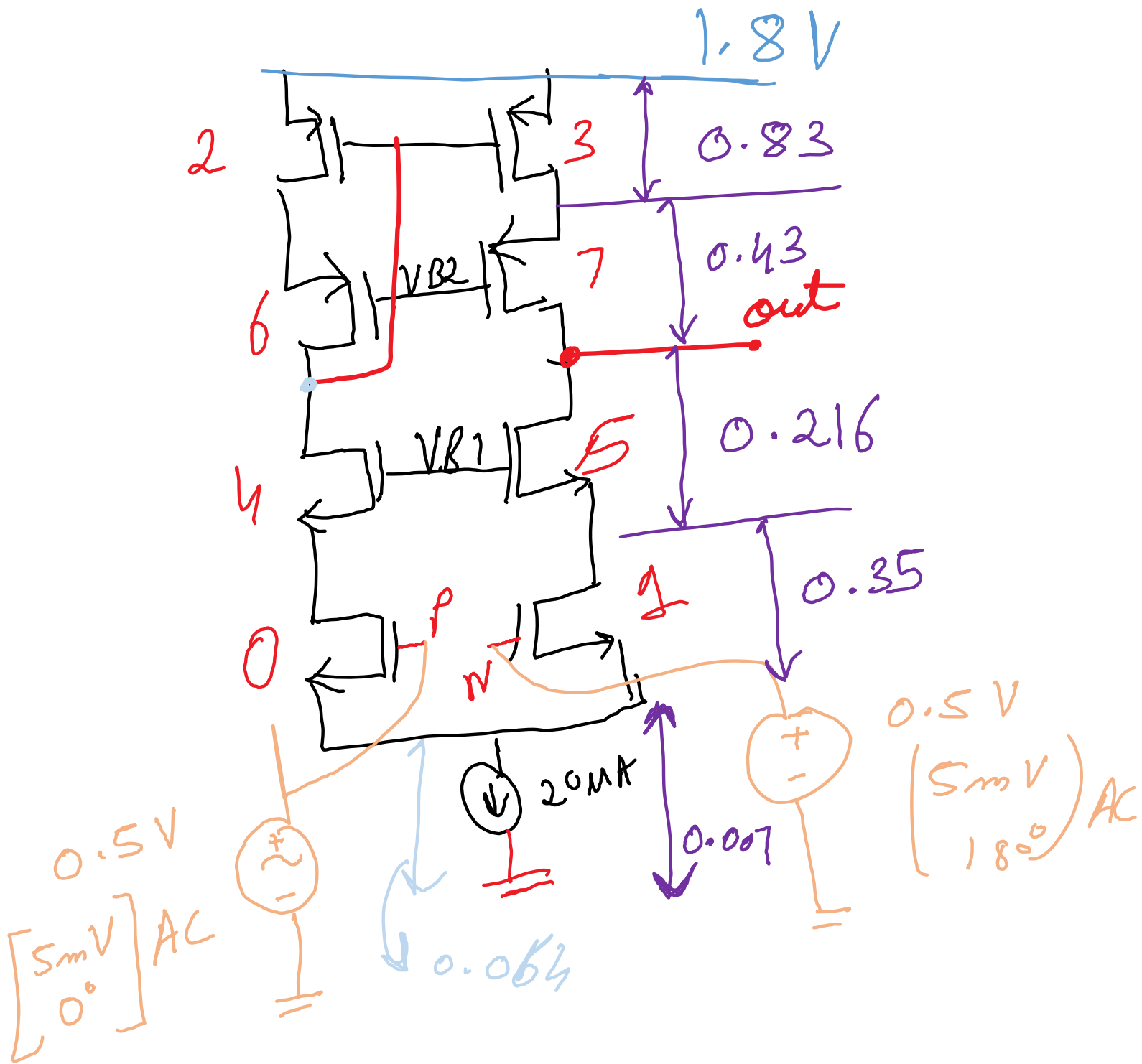
$$\textcircled{1} g_{m0} = \frac{2A I_D}{V_{gs} - V_T} = \frac{2A \times 10.38}{0.5 - 0.392}$$
$$= 0.2ms$$



① Assumed values of V_{DS} for all MOS
(Sat)

① 0.2 1 $V_{DS} = 0.4$

② 1 4 5 $V_{DS} = 0.2$

③ 6 2 7 $|V_{DS}| = 0.5$

④ 2 2 ③ $|V_{DS}| = 0.7$

$$(V_{DS})_{sat} = (V_{GS} - V_{th})$$

As $I = \text{fixed}$, $(V_{GS} - V_{th}) \Rightarrow \text{Assumed}$

and for fixed $L = 1 \mu m$, $V_{th} = 0.4 V$

So $\left(\frac{W}{L}\right)$ is calculated for all of the MOS

① Slew rate

$$= \frac{2I_0}{C_L} = \frac{2 \times 20}{1p} = 40 \times 10^{+12} \times 10^6 = 40 \times 10^6 \text{ V/s}$$

Simulated result = $8.67 \times 10^6 \text{ V/s}$

reason: more MOS so more junction
Cap $C \uparrow$ Slew rate \downarrow

② $UGB = 16 \text{ MHz} - 17 \text{ MHz}$

reason $UGB = \frac{1}{\omega_{out} \times C_L}$

$\Rightarrow \omega_{out} = g_{m3} \parallel g_{m5} \parallel g_{m7} \parallel g_{m8} \parallel g_{m9} \parallel g_{m10}$
 $\Rightarrow = 1.4 \text{ M}\Omega$

$$V_{GB} = \frac{1}{1.4 \text{ M} \times 10^{-12}}$$

$$= \boxed{7.1 \text{ M}\Omega}$$

Calculated

(3)

$$\text{gain} = 0.2 \text{ m} \times 1.4 \text{ M}$$

$$= 48.94 \text{ dB}$$

(4) input referred noise

$$\Rightarrow \frac{16KT}{3g_{m0}} + \frac{16KT}{3g_{m0}^2} \times g_{m7}$$

$$= \frac{16 \left[\frac{1.38 \times 10^{-23} \times 300}{3 \times 0.14} \right] + \frac{16 \times 1.38 \times 10^{-23} \times 300}{3 \times (0.14)^2} \times 0.045}{1}$$

$$\approx 1.577 \times 10^{-16} \text{ V}^2/\text{Hz}$$

$$\begin{aligned} \text{Power} &= 1.577 \times 10^{-16} \times V^2 \times 24 \text{ K} \\ &= 3.78 \times 10^{-11} V^2 \end{aligned}$$

So, we can see that from simulation

$$7.6 \times 10^{-10} V^2$$

So difference is due to other MOS as C-load make path for other model noise to flow.

So From matlab calculated the SNR

$$Fr/Fs=M/N$$

Assuming $M=7$, $N=64$ and $Fs=24 \times 2=48K$ so $Fr=5.25k$

```
close all;
clear all;
clc;
fs = 48000;
data_in_raw=csvread('analogf1m.csv',2);
data_in_raw = data_in_raw(:,2);
nfft = 64;
psd=pwelch(data_in_raw(1:nfft),hann(nfft,'periodic'),1,nfft,fs);
psd_new = psd/max(psd);
semilogx([1:(fs)/(nfft):fs/2]*1e-3,10*log10(psd_new(1:nfft/2)),'LineWidth',2);
hold on;
signal_bin = find(psd_new==max(psd_new(3:nfft/2)));
sig_power = psd_new(signal_bin-1)+psd_new(signal_bin)+psd_new(signal_bin+1);
noise_sum=0;
for k=3:nfft/2
    noise_sum = noise_sum+ psd_new(k);
end
noise_power= noise_sum - sig_power;
snr = 10*log10(sig_power/noise_power);
display(snr);
```

